

$$V_3 = \frac{R_4}{R_3 + R_4} (V_1 - V_0)$$



$$V_1 = A(V_3 - 2.5) = \begin{cases} V_{\max} & ; \quad V_3 > \frac{V_5}{2} \\ V_{\min} & ; \quad V_3 < \frac{V_5}{2} \end{cases}$$


—f—


$$i(t) = C \frac{d(V(t))}{dt}$$

↓
Integrator

$V_{\max} \rightarrow - \text{Ramp}$

$V_{\min} \rightarrow + \text{Ramp}$

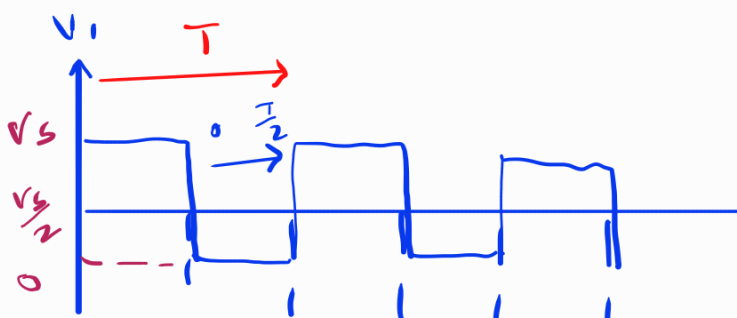

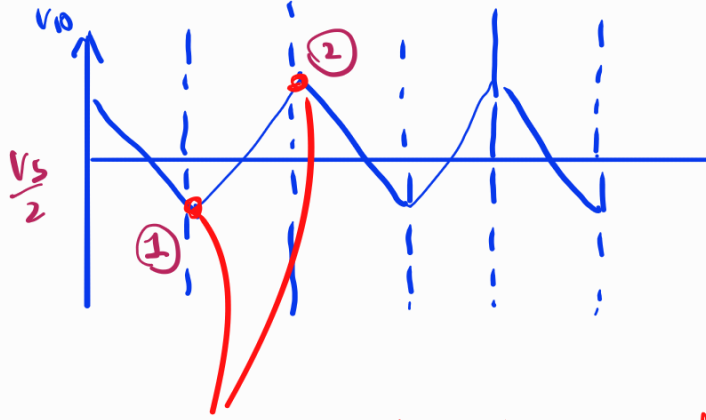

In these points, if we calibrate $V_3 =$
 after that V_3 can be higher or lower than
 Then comparator will be saturate according to that value.

Node at V_3

$$I_1 = I_2 + (I_B) \approx 0$$

$$I_1 = I_2$$

$$\frac{V_o - V_3}{R_4} = \frac{V_3 - V_1}{R_3}$$

for point ①

In just before moment

$$V_1 = V_s \quad V_3 = \frac{V_s}{2}$$

$$\frac{V_o - \frac{V_s}{2}}{R_4} = \frac{\frac{V_s}{2} - V_s}{R_3}$$

$$V_o = \frac{R_4}{R_3} \left(-\frac{V_s}{2} \right) + \frac{V_s}{2}$$

for point ②

just before switching



$$V_1 = 0 \quad V_3 = \frac{V_s}{2}$$

$$\frac{V_o - \frac{V_s}{2}}{R_4} = \frac{\frac{V_s}{2} - 0}{R_3}$$

$$V_o \text{ peak} = \frac{R_4}{R_3} V_s$$

$$V_o = \frac{R_4}{R_3} \left(\frac{V_s}{2} \right) + \frac{V_s}{2}$$

For integrator circuit

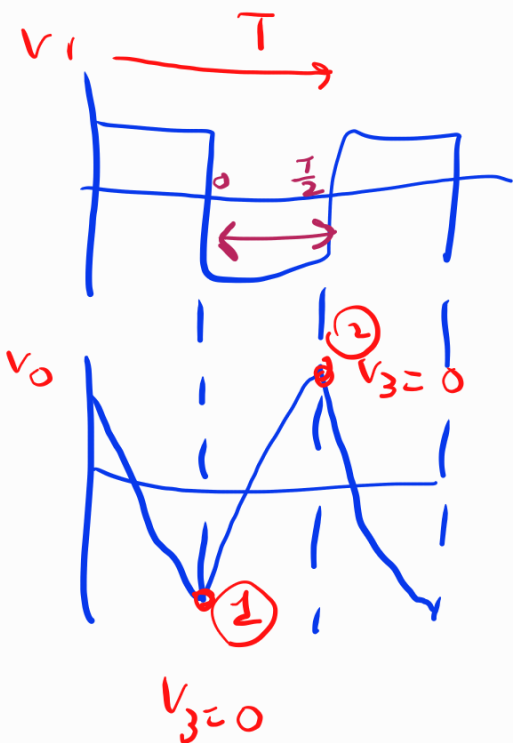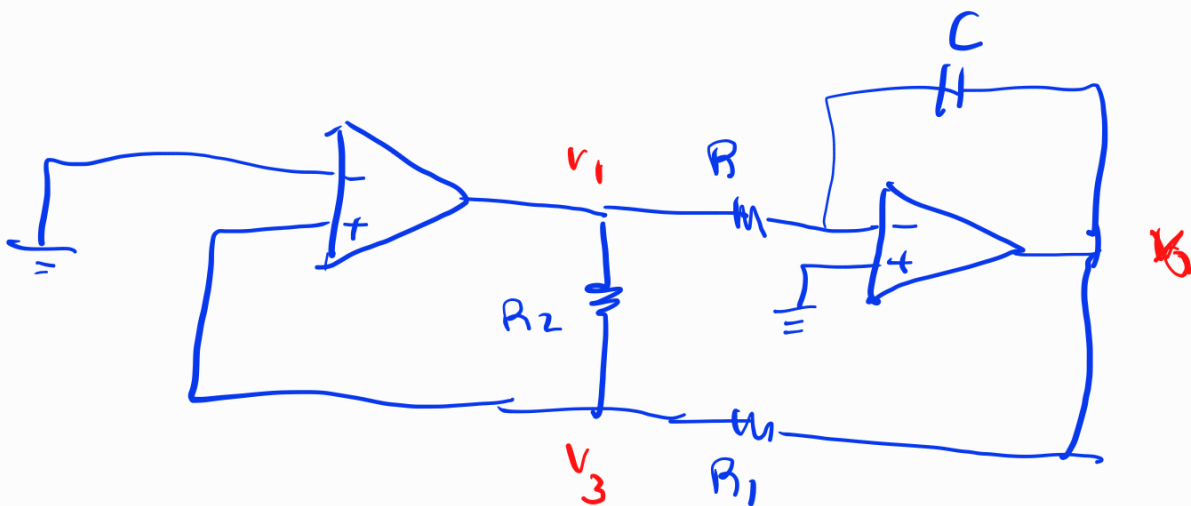

$$\frac{V_0 - V_3}{R_1} = \frac{V_3 - V_1}{R_2}$$

at ①

$$\frac{V_0}{R_1} = -\frac{V}{R_2}$$

$$V_0 = -\frac{R_1}{R_2} V$$

②

$$\frac{V_0}{R_1} = \frac{V}{R_2}$$

$$V_0 = \frac{R_1}{R_2} V$$

$$V_{O_{pk-pk}} = \frac{2R_1}{R_2} V$$

$$V_C = \frac{1}{RC} \int V_i dt$$

$$0 - V_0 = \frac{1}{RC} \int V_i dt$$

$$V_0 = -\frac{1}{RC} \int V_i dt$$

$$V_{O_{pk-pk}} = -\frac{1}{RC} \int_0^{\frac{T}{2}} -V dt$$

$$\frac{2R_1 V}{R_2} = + \frac{1}{RC} \frac{T}{2}$$

$$T = \frac{4 R_1 RC}{R_2}$$

$$f = \frac{R_2}{4 R_1 RC}$$

$$\frac{100 \text{ k}}{4 (47 \text{ k}) (15 \text{ k}) (20 \text{ n})}$$

$$= 354.6$$

$$\frac{100}{4 \times 47 \times 15 \times 0.1} \text{ k}$$

$$= 354.6$$

$$T = 2.8 \text{ ms}$$

$$\approx 3 \text{ ms}$$