

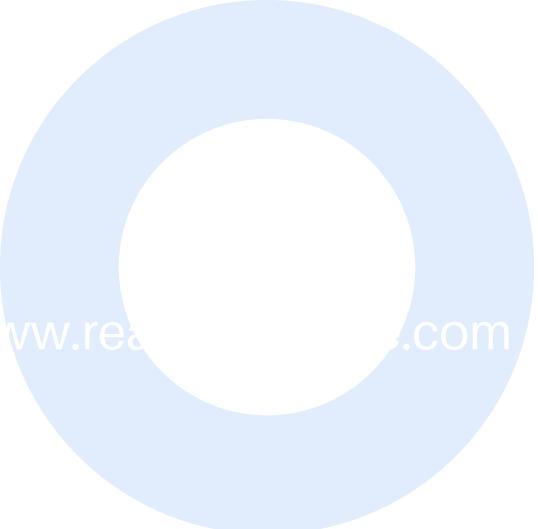


# **ANALOG LINE FOLLOWING ROBOT**


**Presented by Outlaws**

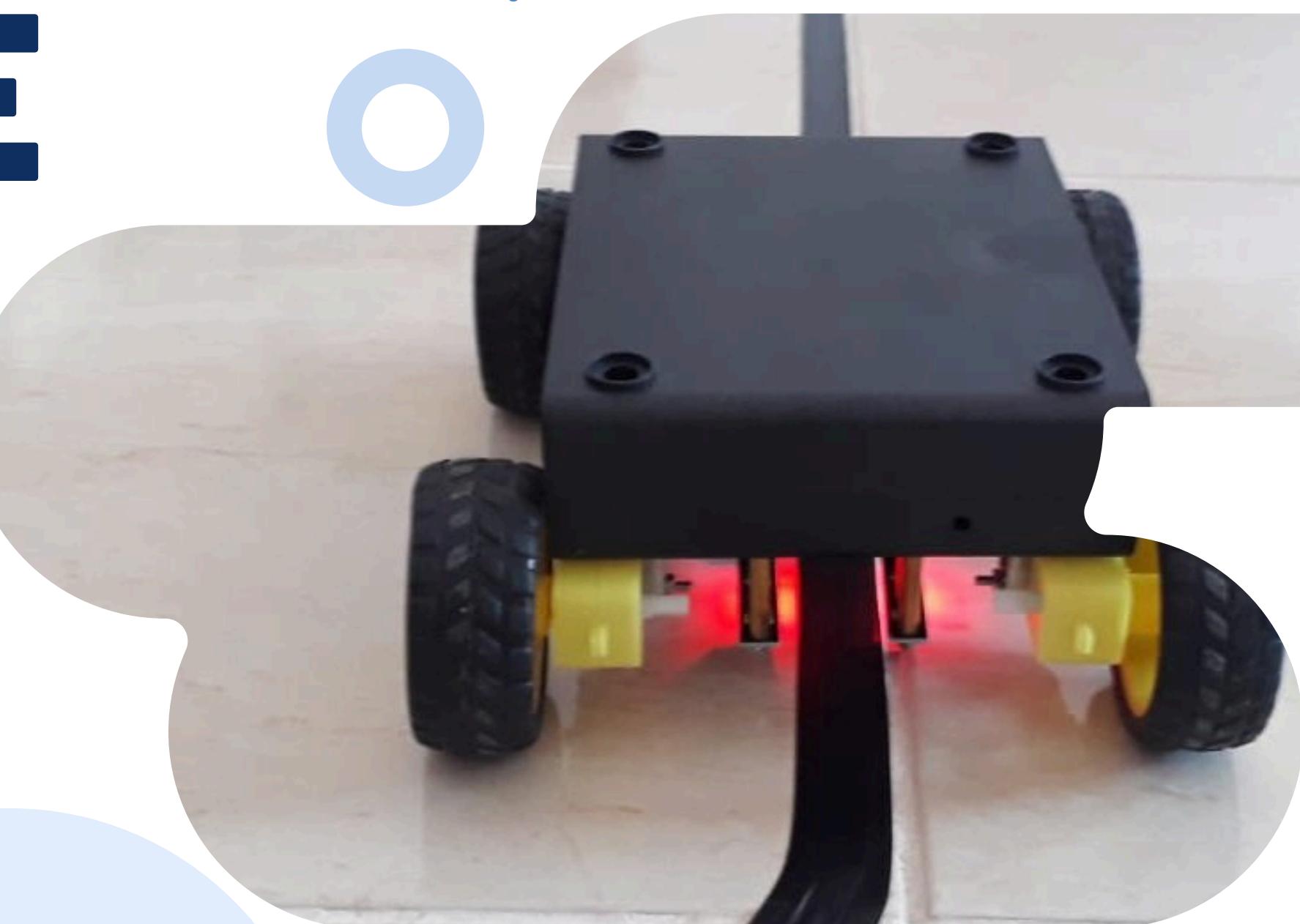

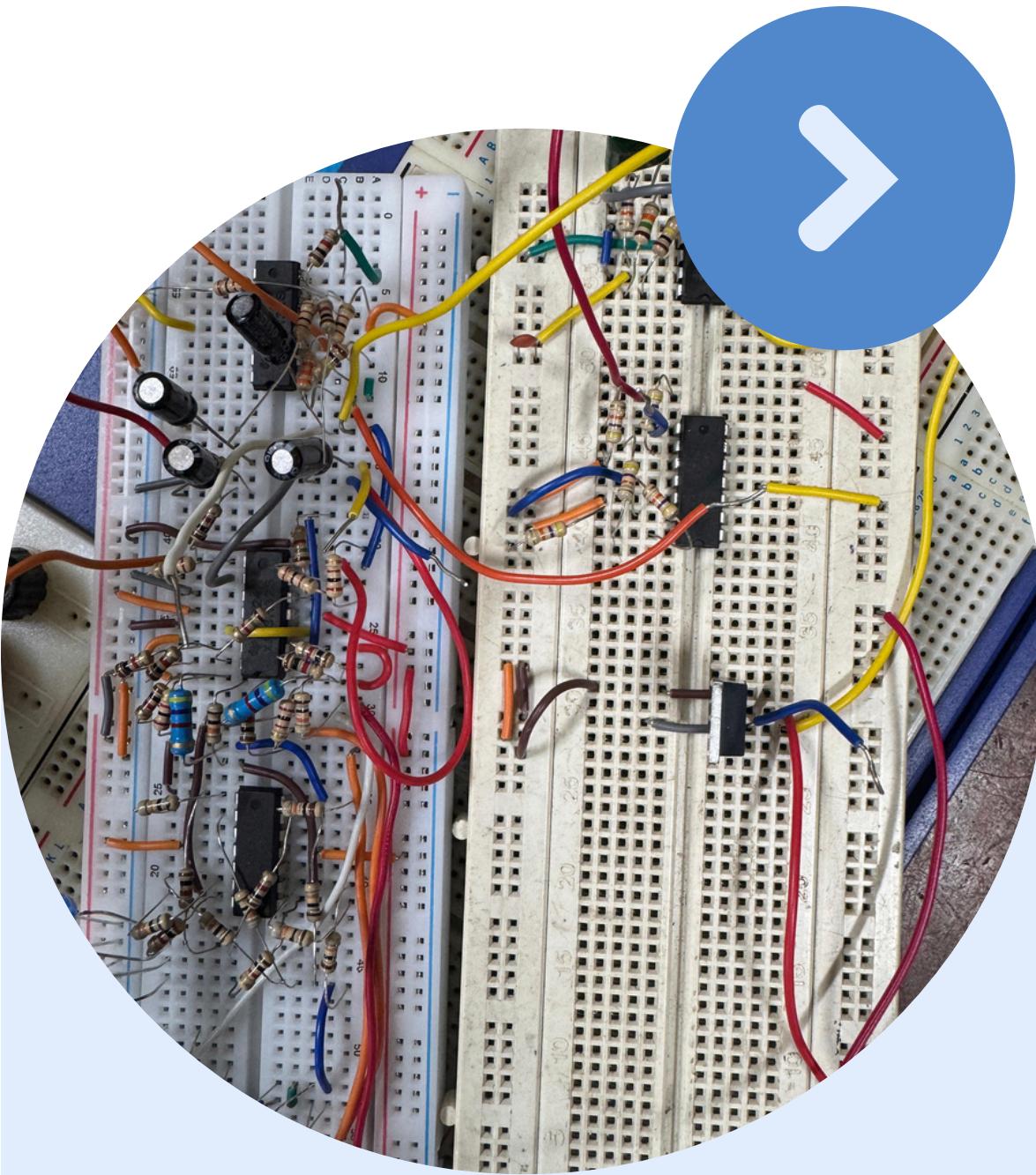
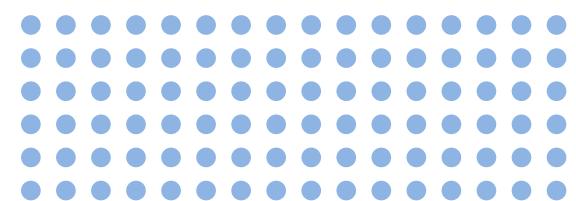
# Project Overview

- Fully analog line-following robot using PID control.
- IR sensor array detects line position.
- Analog circuits generate error and implement PID.
- Comparator with triangular wave produce PWM for motor control.
- Transistors drive motors for smooth, real-time line tracking.



# Components and Selection >>>

## LM324N Op-Amp IC

Contains 4 op-amps in total. Ideal for implementing P, I, D circuits and signal conditioning.

## Capacitors

Used for filtering, integration, and differentiation circuits.

## Voltage Regulators

Used to create a regulated  $\pm 5$  V dual power supply for stable analog operation.

## IR Sensors

Provides accurate line position detection. Analog output simplifies processing.

## Resistors & Variable resistors

Used for setting PID gains ( $K_p, K_i, K_d$ ) and voltage division.

## DC Motors

Provide motion to the robot and respond effectively to PWM control signals.


## 3.7 V Li-ion Batteries

Used as the main power source. Two batteries connected in series supply sufficient voltage for both regulators to produce  $\pm 5$  V.

## MOSFETs

Used as efficient electronic switches for driving DC motors with PWM signals. Offer fast switching speed and low power loss compared to BJTs.

# System Block Diagram

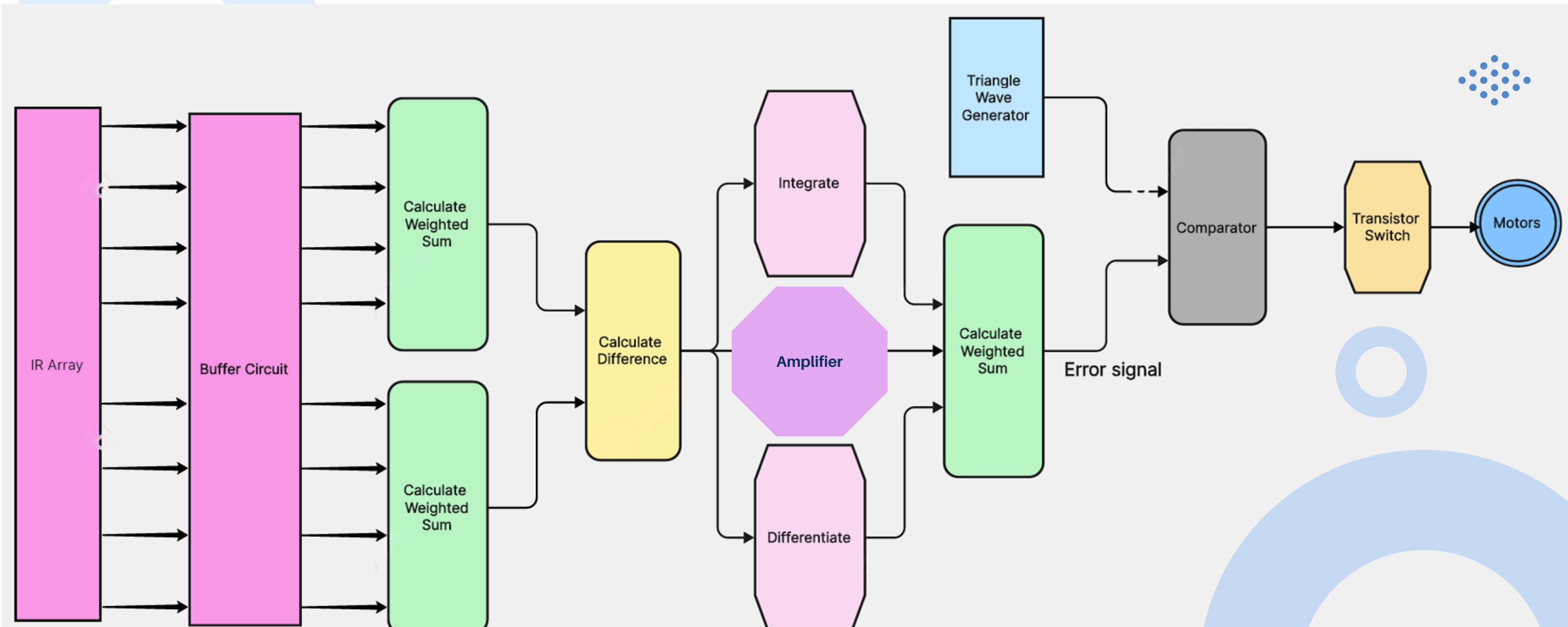

# Functionality

## IR Sensor Array


**Function:** Detects the position of the black line on a white surface. Provides analog voltage proportional to reflected light intensity.

**Component:** 8 IR emitter-receiver pairs.

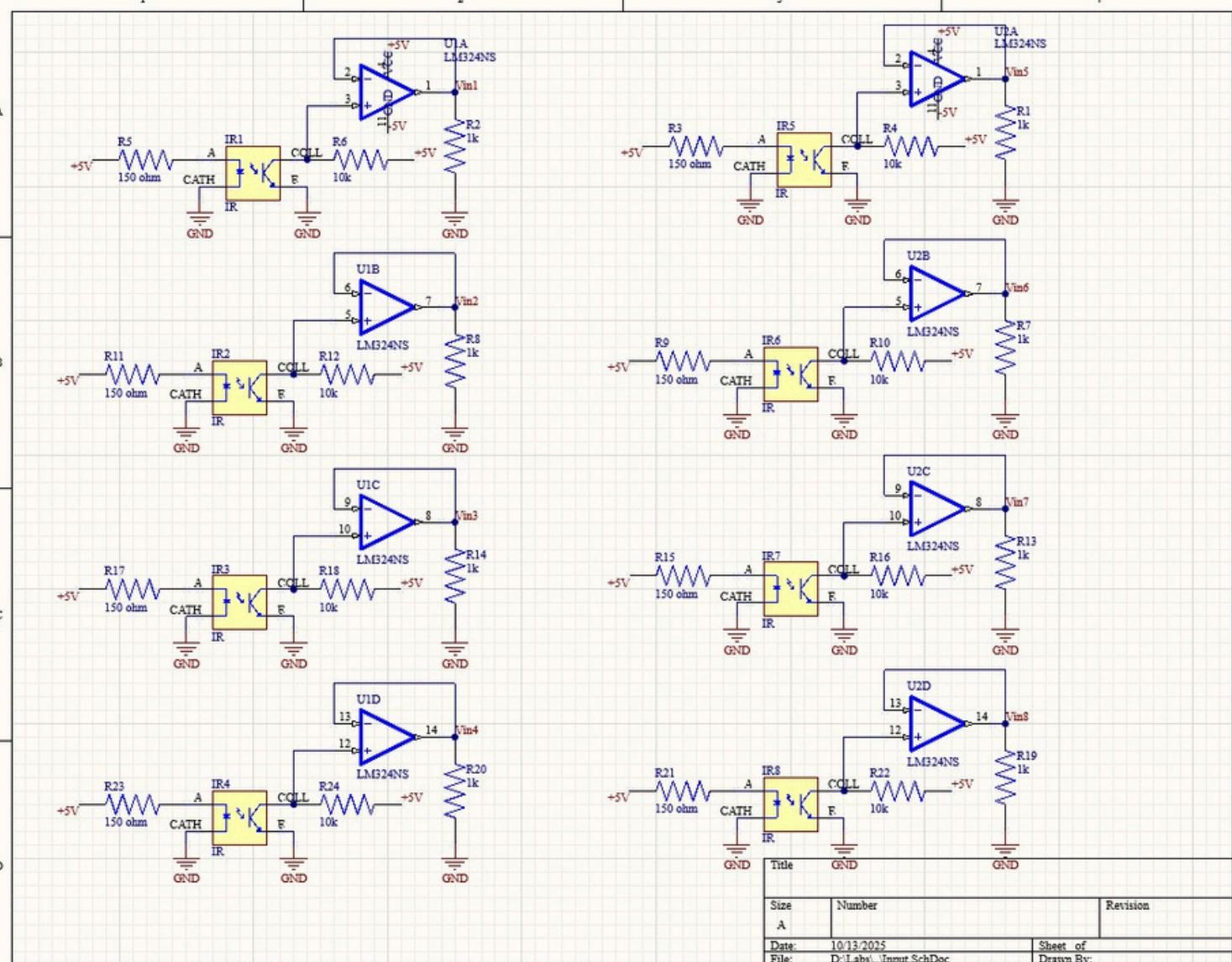
## Buffer Circuit

**Function:** Isolates the sensor array from the next stage and prevents signal interference.

**Component:** Op-amps from LM324 in voltage follower mode.



Input IR sensors and buffers

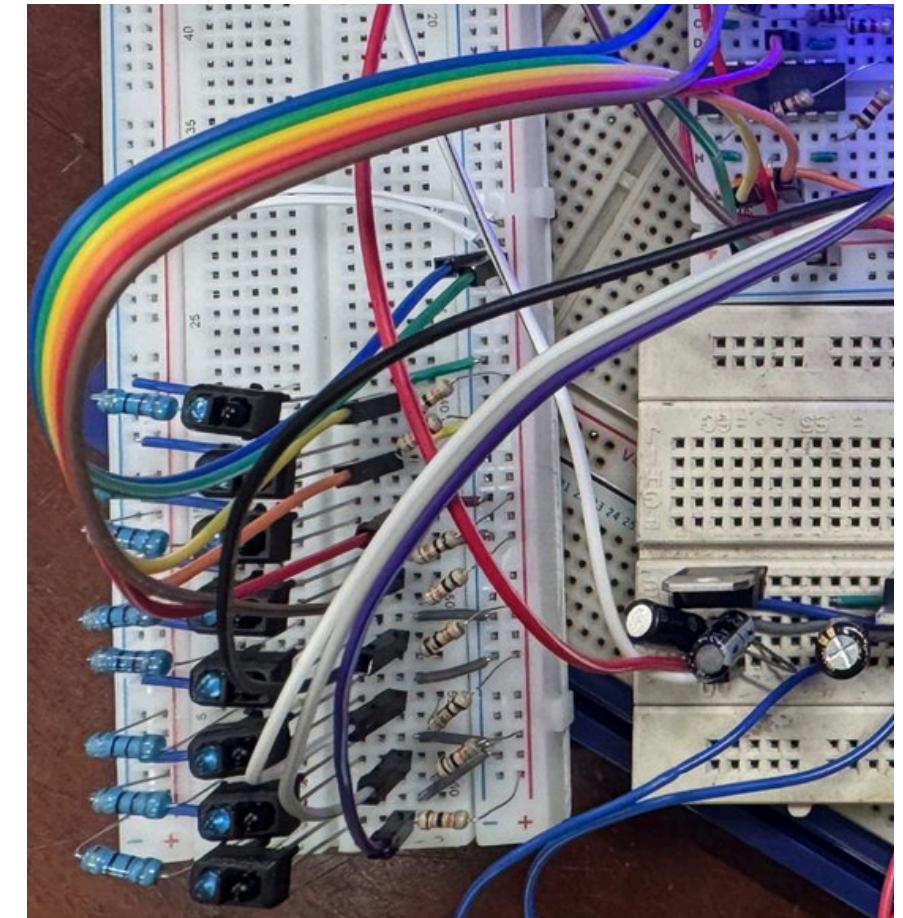

# Functionality

## Weighted Sum Calculation


**Function:** Computes position information by giving different weights to each sensor.

**Component:** Scaling adder circuit using op-amps and resistors.

## Calculate Difference

**Function:** Produces the error signal by comparing left and right sums.

**Component:** Differential amplifier

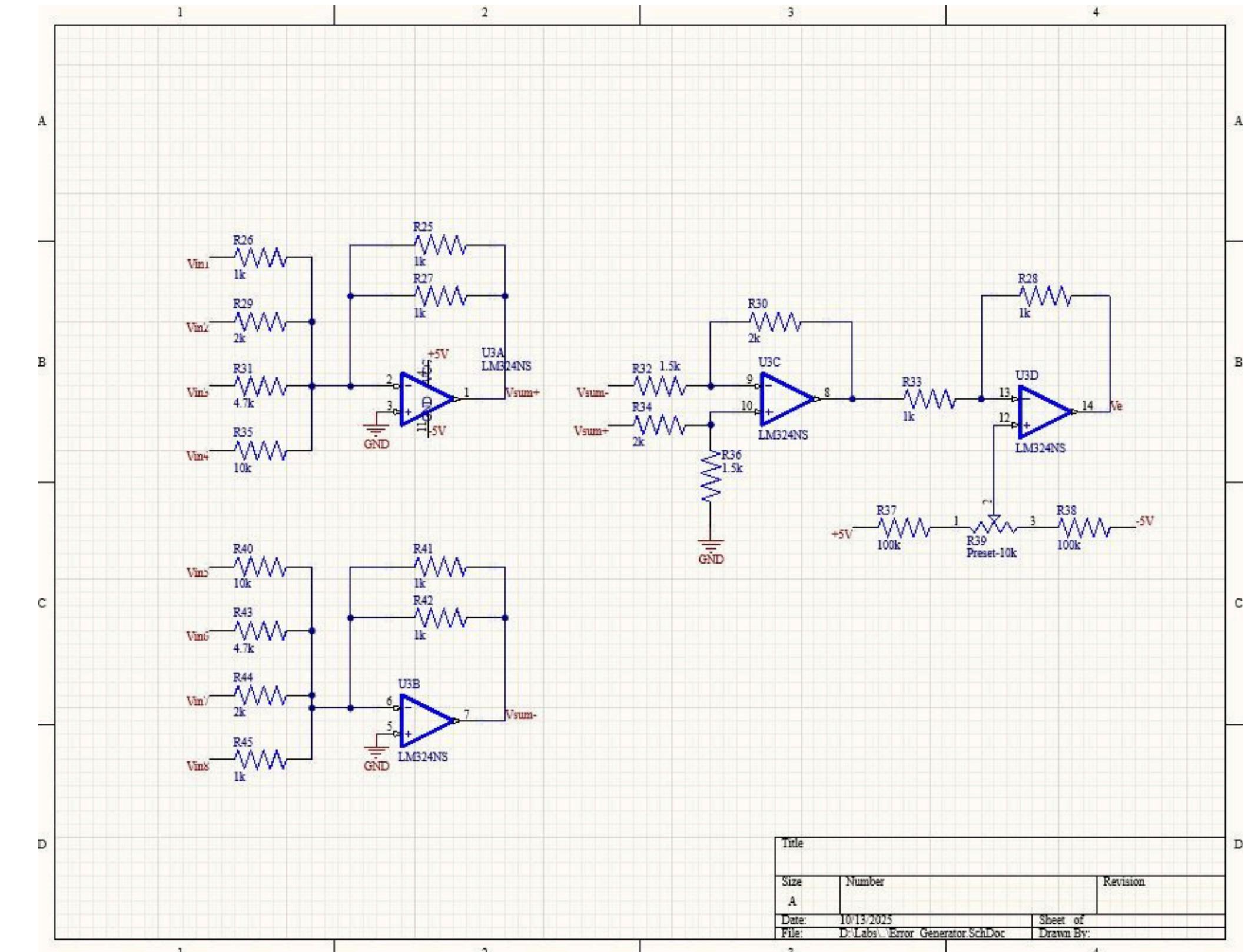


Scaling adders and Subtractor

# Functionality
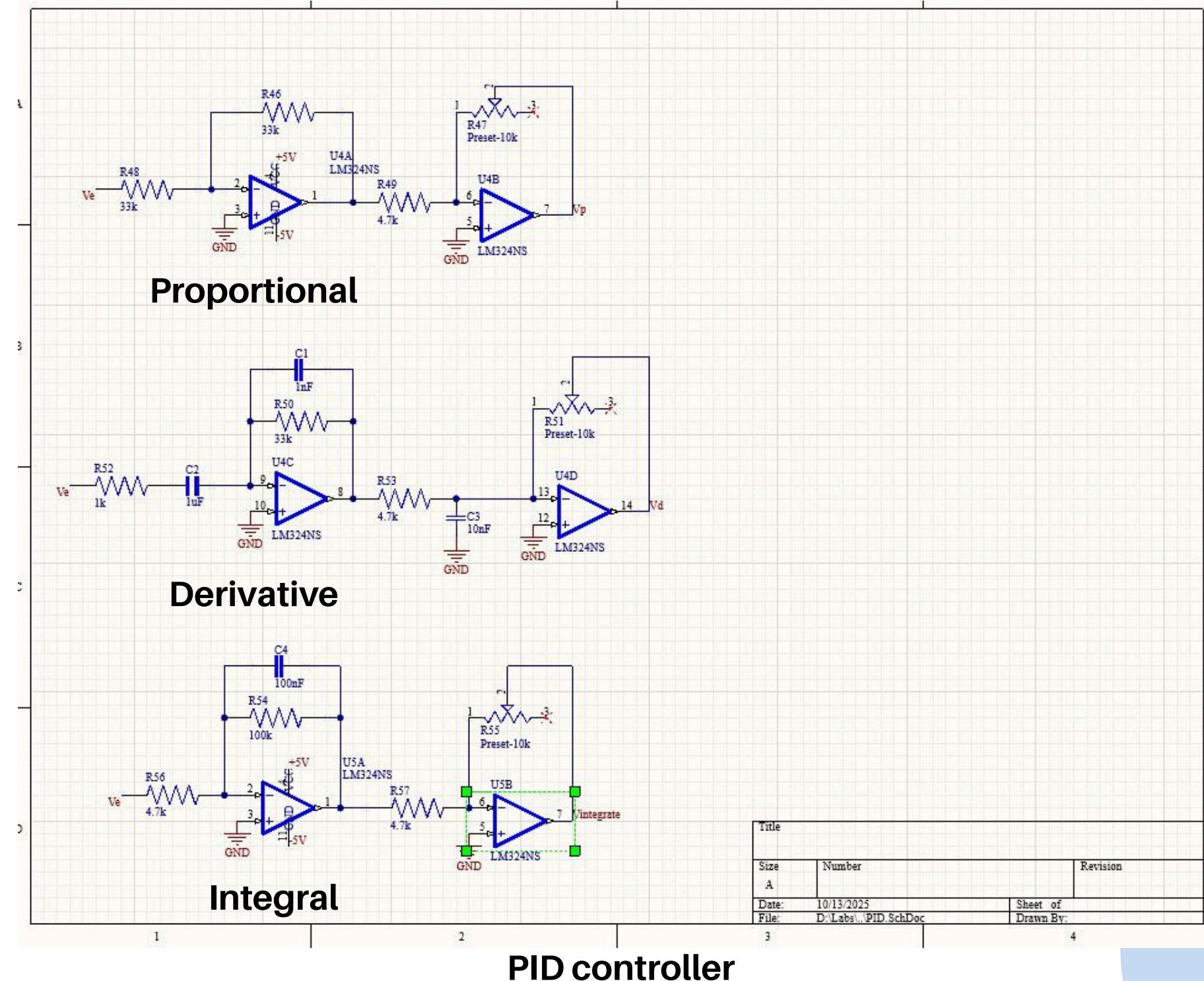
## PID Control

- **Proportional (P):** Directly amplifies error signal.
  - Provides immediate correction proportional to error.
- **Integral (I):** Integrates error over time using an op-amp integrator.
  - Eliminates steady-state error.
- **Derivative (D):** Differentiates error signal using an op-amp differentiator.
  - Predicts and reduces overshoot.



# Functionality

## Transistor Switch


**Function:** Drives DC motors based on PWM signal.

**Component:** Power transistors

## Motors

**Function:** Execute movement and correction.

**Component:** Two DC gear motors.

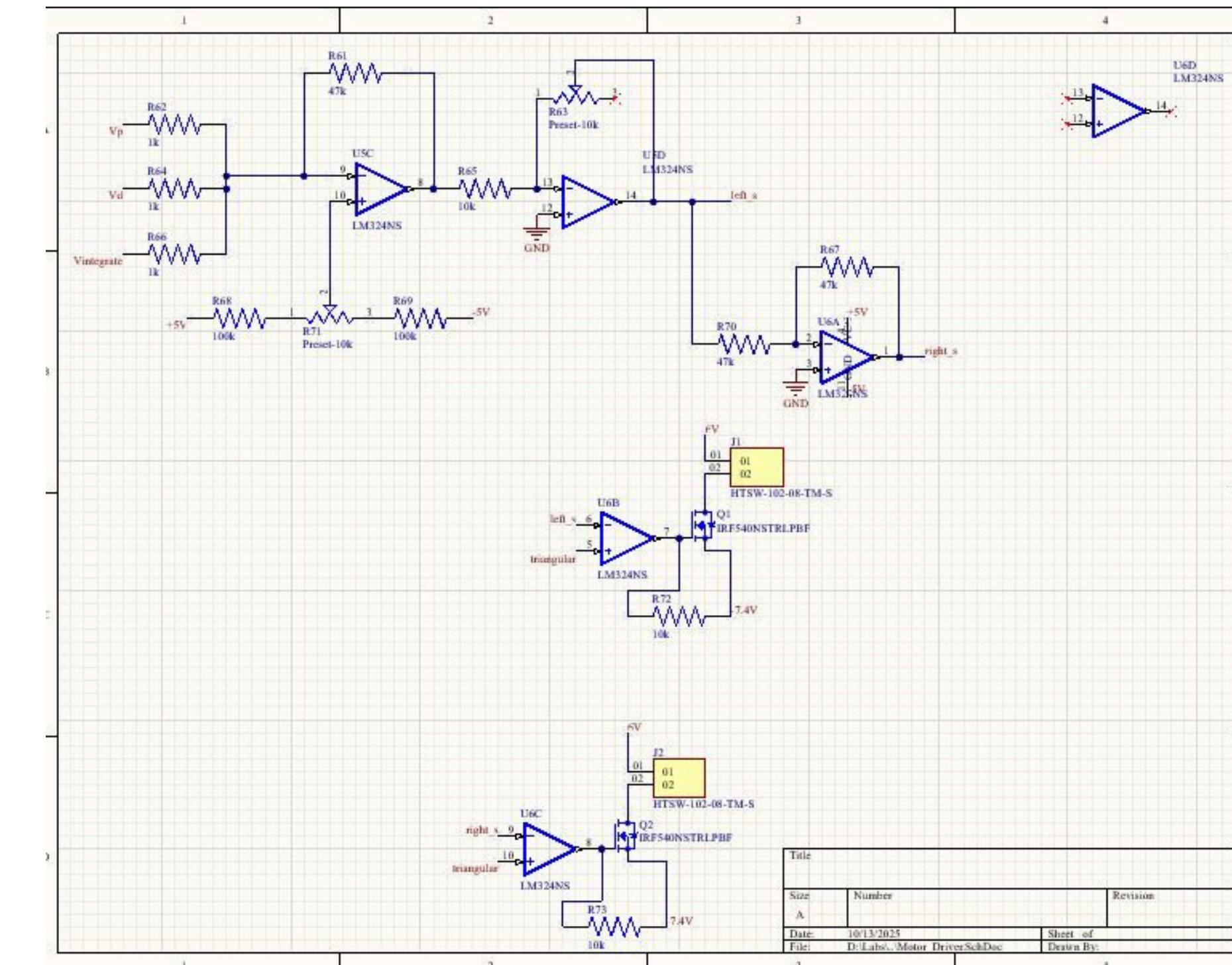

Motor controlling circuit

# Functionality

## Triangle Wave Generator


**Function:** Produces a periodic triangle waveform.

**Component:** Op-amp-based integrator + comparator.

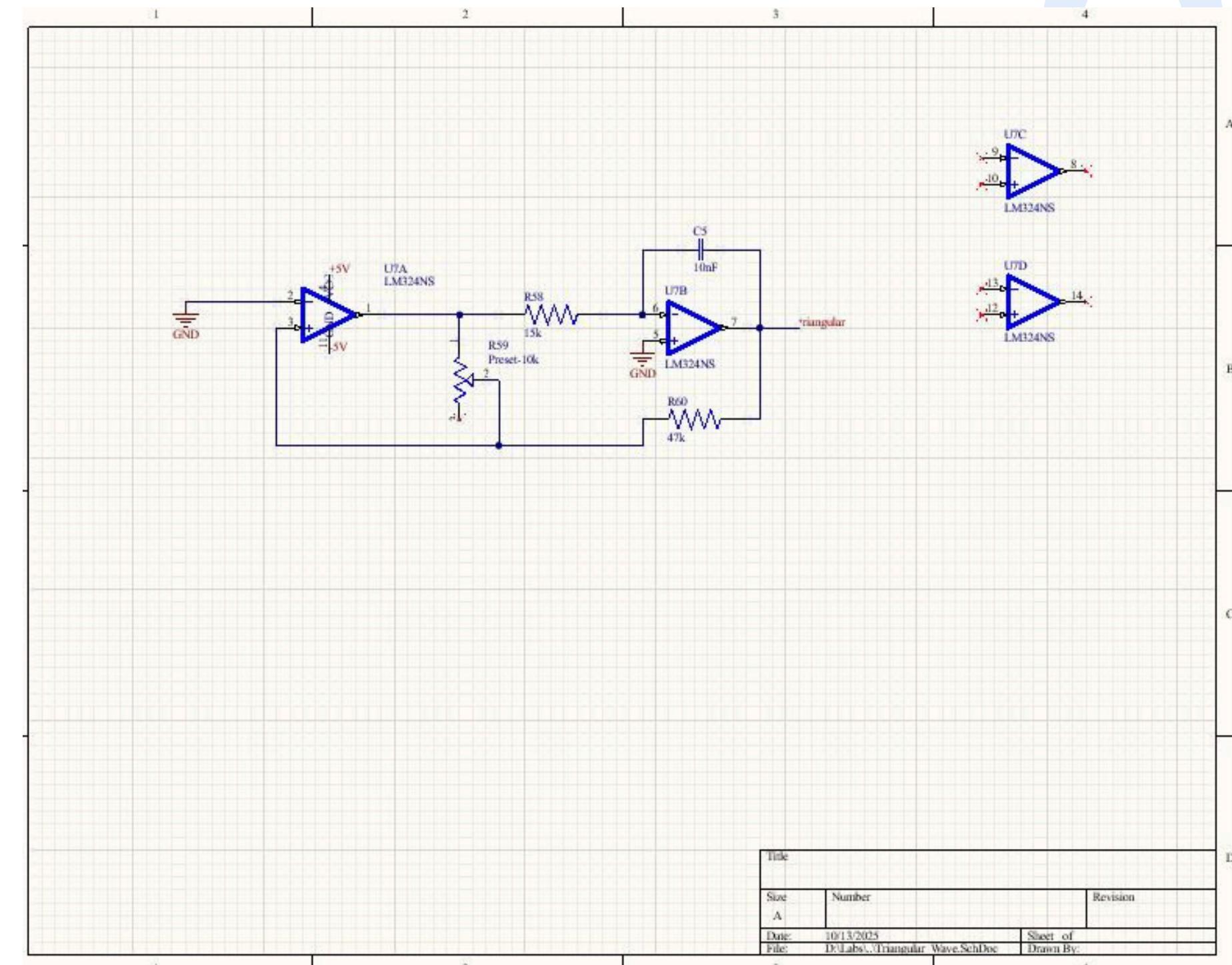
## Comparator

**Function:** Compares PID output with triangle wave to generate PWM.

**Component:** Op-amp in comparator mode.





Triangular wave generator

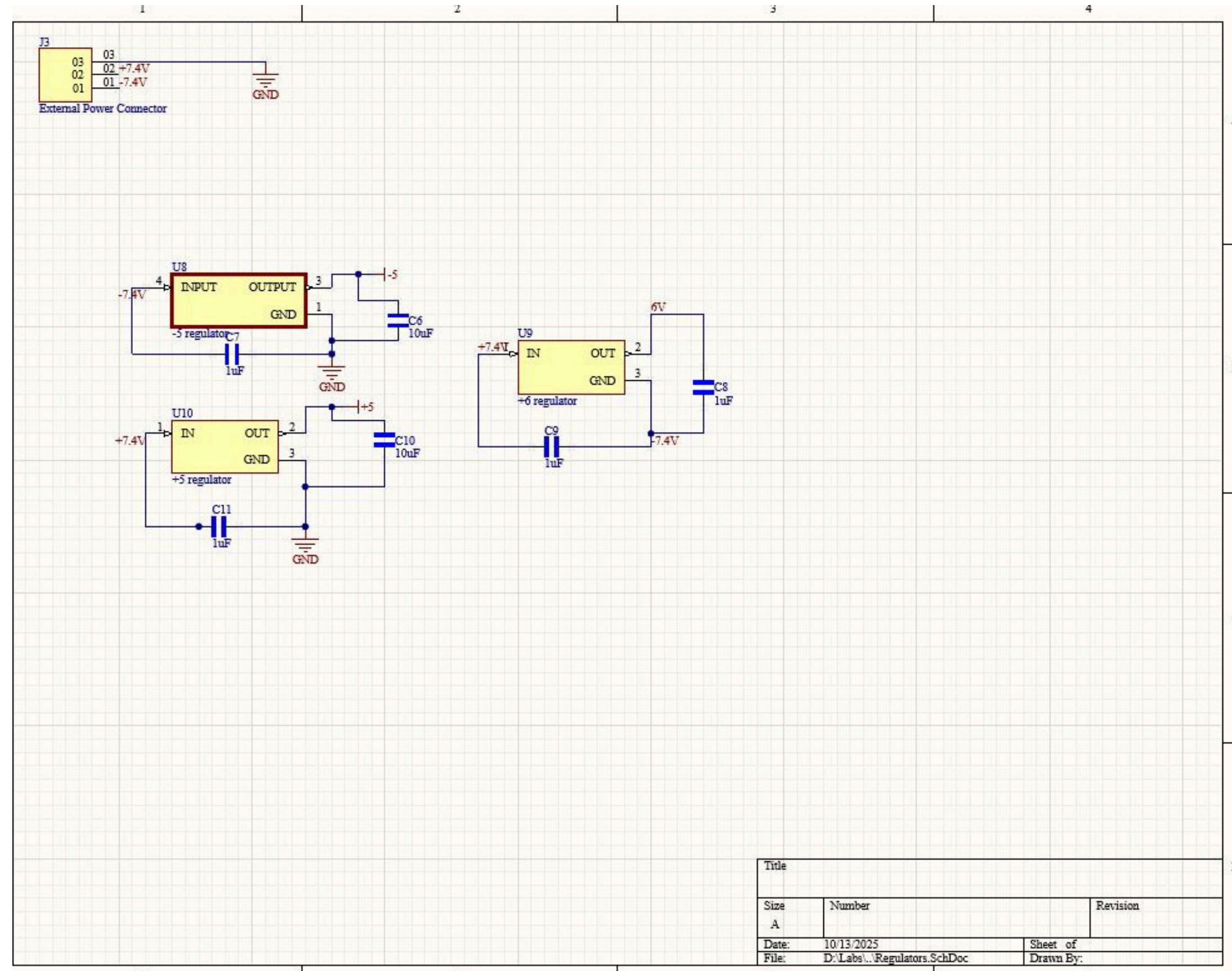



## Regulators and power management circuits



# PCB Design

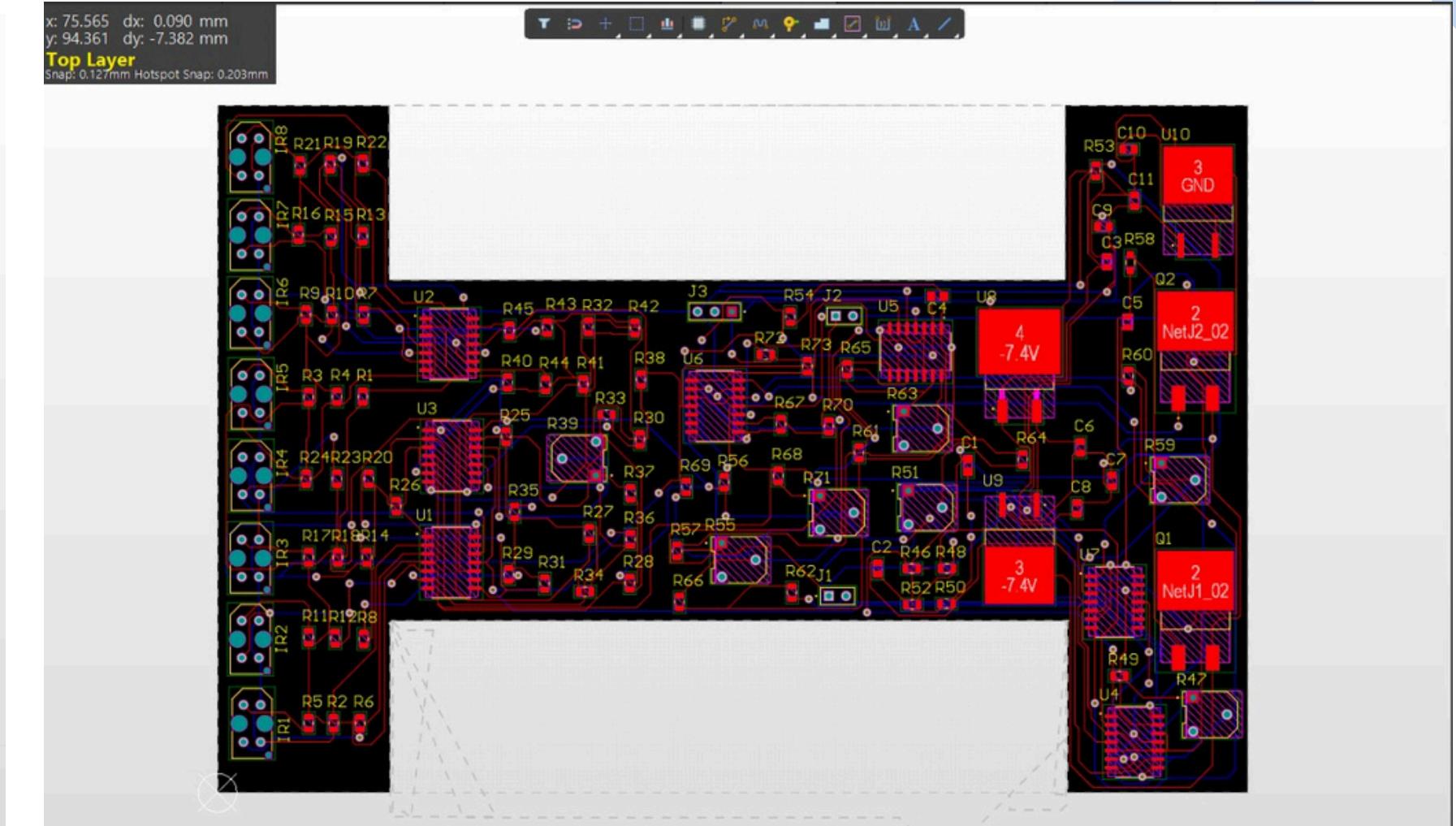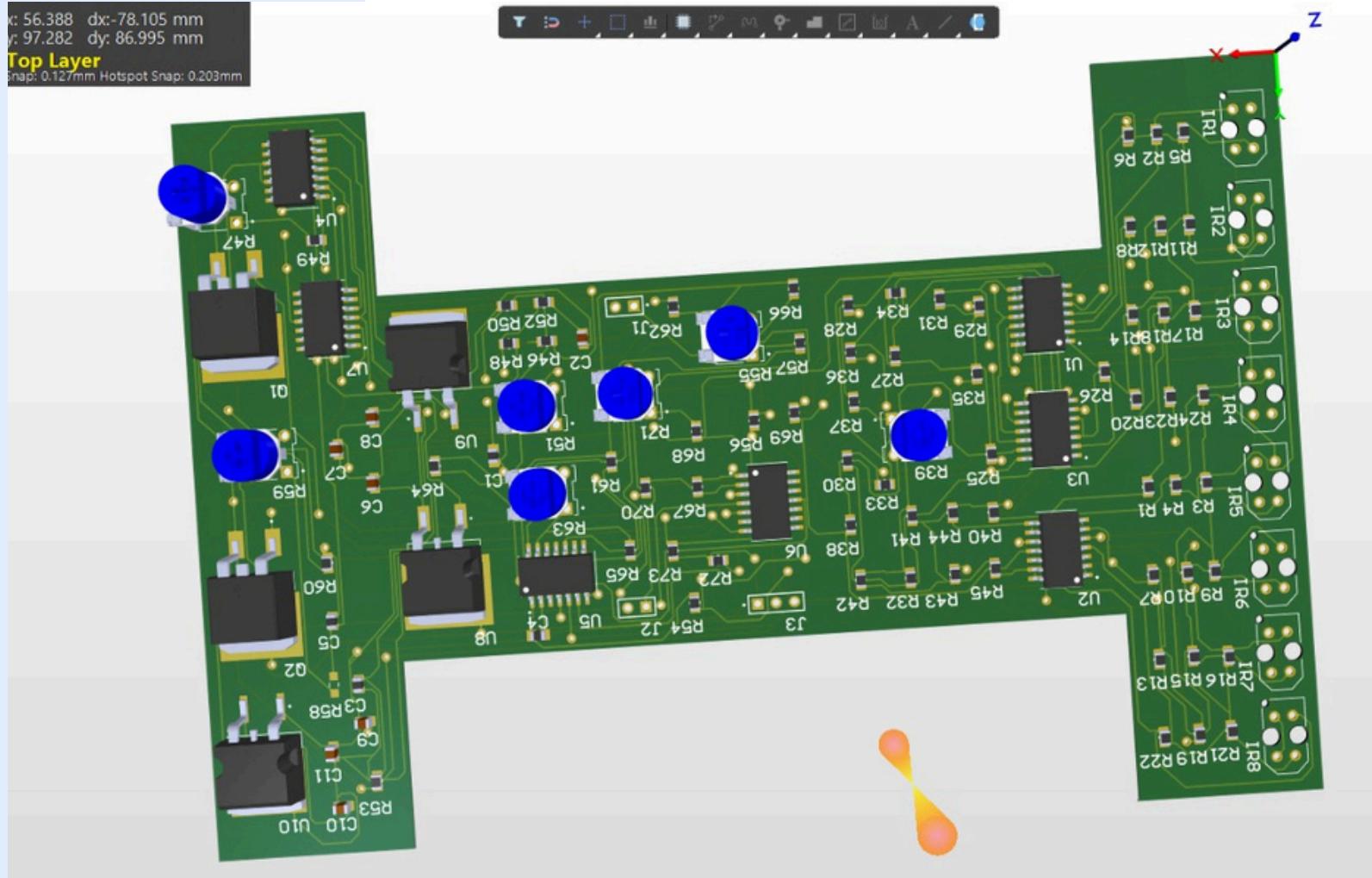

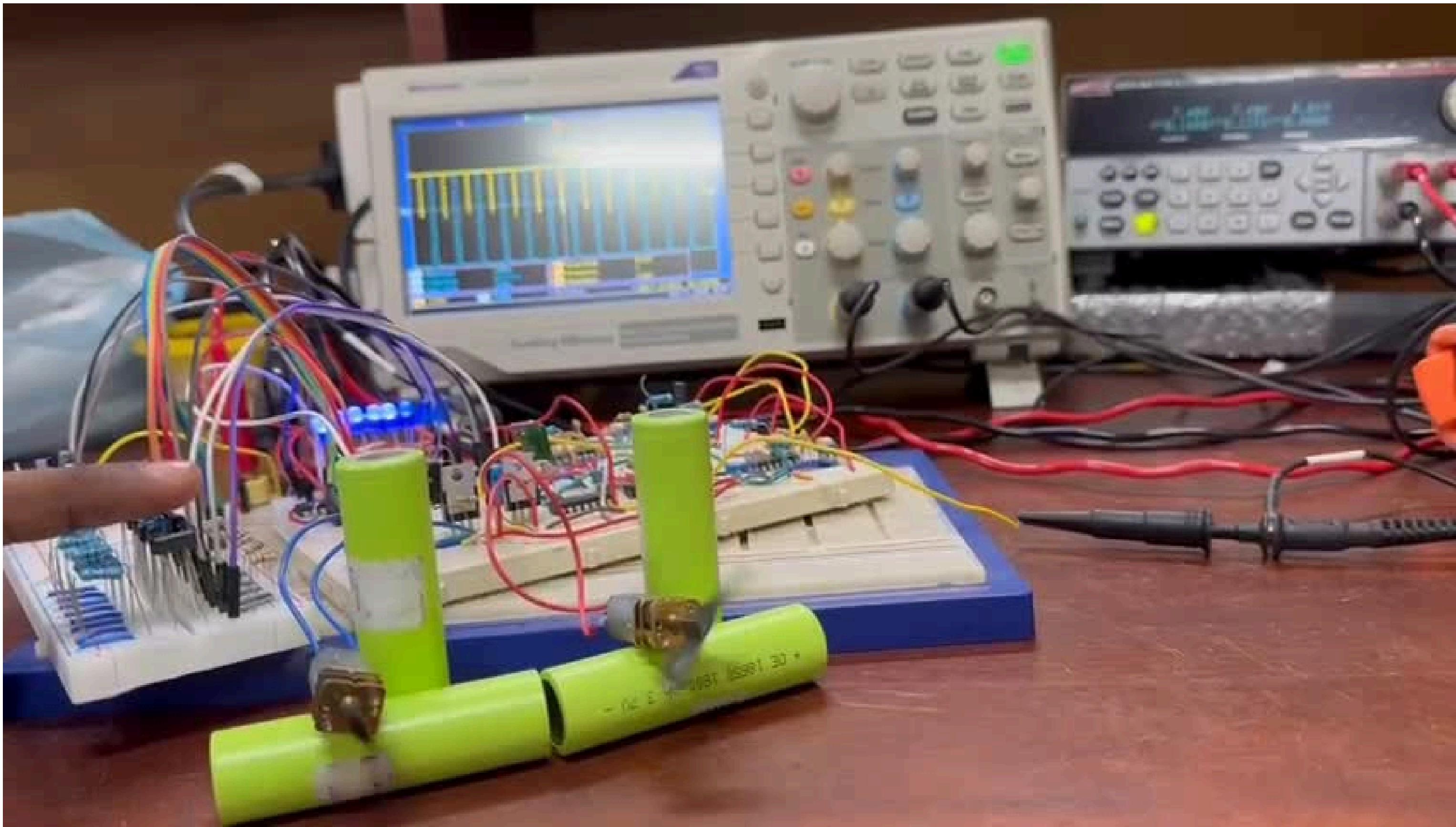

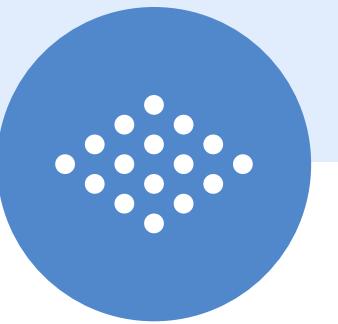

**THANK  
YOU!**

